

Lógica Digital (1001351)

Síntese lógica

Prof. Edilson Kato

kato@ufscar.br

Prof. Maurício Figueiredo

mauricio@ufscar.br

Prof. Ricardo Menotti

menotti@ufscar.br

Prof. Roberto Inoue

rsinoue@ufscar.br

Departamento de Computação
Universidade Federal de São Carlos

Atualizado em: 29 de março de 2019



Síntese Lógica

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$


$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$

$$f(x_1, x_2) = 1.x_2 + \bar{x}_1.1$$


$$f(x_1, x_2) = x_2 + \bar{x}_1$$

Figure 2.19 A function to be synthesized.

Síntese Lógica

 


(a) Canonical sum-of-products

 

(b) Minimal-cost realization

Figure 2.20 Two implementations of the function in Figure 2.19.

Síntese Lógica

 

(a) Conveyor and sensors

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b) Truth table

$$\begin{aligned} & \bar{s}_1 \bar{s}_2 s_3 + \bar{s}_1 s_2 s_3 + s_1 \bar{s}_2 s_3 + s_1 s_2 s_3 + s_1 s_2 \bar{s}_3 + s_1 s_2 s_3 \\ & \bar{s}_1 s_3 (\bar{s}_2 + s_2) + s_1 s_3 (\bar{s}_2 + s_2) + s_1 s_2 (\bar{s}_3 + s_3) \\ & \bar{s}_1 s_3 + s_1 s_3 + s_1 s_2 \\ & s_3 + s_1 s_2 \end{aligned}$$

ou

$$\begin{aligned} & \bar{s}_1 \bar{s}_2 s_3 + \bar{s}_1 s_2 s_3 + s_1 \bar{s}_2 s_3 + s_1 s_2 s_3 + s_1 s_2 \bar{s}_3 + s_1 s_2 s_3 \\ & s_3 (\bar{s}_1 \bar{s}_2 + \bar{s}_1 s_2 + s_1 \bar{s}_2 + s_1 s_2) + s_1 s_2 (\bar{s}_3 + s_3) \\ & s_3 \cdot 1 + s_1 s_2 \\ & s_3 + s_1 s_2 \end{aligned}$$

ou

$$\begin{aligned} & \bar{s}_1 \bar{s}_2 s_3 + \bar{s}_1 s_2 s_3 + s_1 \bar{s}_2 s_3 + \bar{s}_1 \bar{s}_2 s_3 + s_1 s_2 \bar{s}_3 + s_1 s_2 s_3 \\ & \bar{s}_1 s_3 (s_2 + \bar{s}_2) + \bar{s}_2 s_3 (s_1 + \bar{s}_1) + s_1 s_2 (\bar{s}_3 + s_3) \\ & \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2 \\ & s_3 (\bar{s}_1 + \bar{s}_2) + s_1 s_2 \\ & s_3 (\overline{s_1 s_2}) + s_1 s_2 \\ & s_3 + s_1 s_2 \end{aligned}$$

$$\begin{aligned} & f(s_1, s_2, s_3) = \\ & \bar{s}_1 \bar{s}_2 s_3 + \bar{s}_1 s_2 s_3 + s_1 \bar{s}_2 s_3 + s_1 s_2 \bar{s}_3 + s_1 s_2 s_3 \end{aligned}$$

Minterms e maxterms

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

Figure 2.22 Three-variable minterms and maxterms.

Formas canônicas

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Figure 2.23 A three-variable function.

Soma dos produtos:

$$f(x_1, x_2, x_3) = \Sigma(m_1, m_4, m_5, m_6)$$

$$f(x_1, x_2, x_3) = \Sigma m(1, 4, 5, 6)$$

Produto das somas:

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$


Formas canônicas

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0


Figure 2.23 A three-variable function.

$$\begin{aligned}\overline{f} &= m_0 + m_2 + m_3 + m_7 \\ f &= \overline{m_0 + m_2 + m_3 + m_7} \\ f &= \overline{m_0} \overline{m_2} \overline{m_3} \overline{m_7} \\ f &= M_0.M_2.M_3.M_7\end{aligned}$$

Implementações possíveis para a função

 

 
(a) A minimal sum-of-products realization




(b) A minimal product-of-sums realization

Figure 2.24 Two realizations of the function in Figure 2.23.

Portas NAND e NOR

 


(a) NAND gates

 


(b) NOR gates

Figure 2.25 NAND and NOR gates.

Teorema DeMorgan

 
 
$$(a) \quad \overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$$



$$(b) \quad \overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$$

Figure 2.26 DeMorgan's theorem in terms of logic gates.

Exemplos

 


Figure 2.27 Using NAND gates to implement a sum-of-products.

Exemplos



 


Figure 2.28 Using NOR gates to implement a product-of-sums.

Exemplos

 


(a) POS implementation

 


(b) NOR implementation

Figure 2.29 NOR-gate realization of the function in Example 2.13.

Exemplos

 

(a) SOP implementation

 

(b) NAND implementation

Figure 2.30 NAND-gate realization of the function in Example 2.10.

Bibliografia

- ▶ Brown, S. & Vranesic, Z. - Fundamentals of Digital Logic with Verilog Design, 3rd Ed., Mc Graw Hill, 2009

Lógica Digital (1001351)

Síntese lógica

Prof. Edilson Kato

kato@ufscar.br

Prof. Maurício Figueiredo

mauricio@ufscar.br

Prof. Ricardo Menotti

menotti@ufscar.br

Prof. Roberto Inoue

rsinoue@ufscar.br

Departamento de Computação
Universidade Federal de São Carlos

Atualizado em: 29 de março de 2019

