

# Lógica Digital (1001351)

## Circuitos Sequenciais: Latches e Flip-flops

Prof. Edilson Kato

[kato@ufscar.br](mailto:kato@ufscar.br)

Prof. Maurício Figueiredo

[mauricio@ufscar.br](mailto:mauricio@ufscar.br)

Prof. Ricardo Menotti

[menotti@ufscar.br](mailto:menotti@ufscar.br)

Prof. Roberto Inoue

[rsinoue@ufscar.br](mailto:rsinoue@ufscar.br)

Departamento de Computação  
Universidade Federal de São Carlos

Atualizado em: 11 de maio de 2019




# Objetivos


Nesta aula vamos aprender sobre:

- ▶ Circuitos lógicos que podem armazenar informações;
- ▶ Latches e Flip-flops, os quais armazenam um único bit.
  
# Necessidade


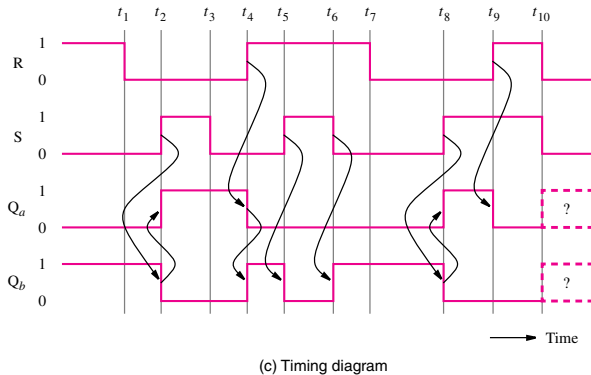


**Figure 5.1** Control of an alarm system.

 


**Figure 5.2** A simple memory element.

# Latch básico



**Figure 5.4** A basic latch built with NOR gates.


# Latch com habilita (*gated latch*)

 

(a) Circuit


Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table

 


(c) Timing diagram

# Latch com habilita (*gated latch*)

 


(c) Timing diagram

 

(d) Graphical symbol


**Figure 5.5** Gated SR latch.

# Latch construído com portas NAND

 

**Figure 5.6** Gated SR latch with NAND gates.


# Latch D

 

(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1


(b) Characteristic table

 

(c) Graphical symbol




# Latch D

 


(d) Timing diagram

**Figure 5.7** Gated D latch.

# Flip-flop D Mestre/Escravo

 


(a) Circuit

 


(b) Timing diagram

# Flip-flop D Mestre/Escravo

 


(b) Timing diagram

 


(c) Graphical symbol

**Figure 5.9** Master-slave D flip-flop.
 
# Flip-flop D com borda positiva (subida)



(a) Circuit

 


(b) Graphical symbol


**Figure 5.11** A positive-edge-triggered D flip-flop.



 
# Flip-flop D Mestre/Escravo com borda positiva



(a) Circuit

 


# Flip-flop T

 


(a) Circuit

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(b) Characteristic table

 


(c) Graphical symbol

 

(d) Timing diagram

**Figure 5.15** T flip-flop.


# Flip-flop JK

 

(a) Circuit

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Characteristic table

 

(c) Graphical symbol

**Figure 5.16** JK flip-flop.



# Bibliografia

- ▶ Brown, S. & Vranesic, Z. - Fundamentals of Digital Logic with Verilog Design, 3rd Ed., Mc Graw Hill, 2009
- ▶ <https://www.falstad.com/circuit/e-nandff.html>

# Lógica Digital (1001351)

## Circuitos Sequenciais: Latches e Flip-flops

Prof. Edilson Kato

[kato@ufscar.br](mailto:kato@ufscar.br)

Prof. Maurício Figueiredo

[mauricio@ufscar.br](mailto:mauricio@ufscar.br)

Prof. Ricardo Menotti

[menotti@ufscar.br](mailto:menotti@ufscar.br)

Prof. Roberto Inoue

[rsinoue@ufscar.br](mailto:rsinoue@ufscar.br)

Departamento de Computação  
Universidade Federal de São Carlos

Atualizado em: 11 de maio de 2019

