

# Lógica Digital (1001351)

## Outros Circuitos Combinacionais

Prof. Edilson Kato

[kato@ufscar.br](mailto:kato@ufscar.br)

Prof. Maurício Figueiredo

[mauricio@ufscar.br](mailto:mauricio@ufscar.br)

Prof. Ricardo Menotti

[menotti@ufscar.br](mailto:menotti@ufscar.br)

Prof. Roberto Inoue

[rsinoue@ufscar.br](mailto:rsinoue@ufscar.br)

Departamento de Computação  
Universidade Federal de São Carlos

Atualizado em: 18 de abril de 2019



# Comparadores

Comparadores

Deslocadores

Comparadores

Deslocadores

ULA

Comparadores

Deslocadores

ULA

Verilog

Comparadores

Deslocadores

ULA

Verilog

Erros comuns

Comparadores

Deslocadores


ULA

Verilog

Erros comuns

Bibliografia

# Comparador

 


**Figure 4.22** A four-bit comparator circuit.



## figure4.40.v

```
1 module compare (A, B, AeqB, AgtB, AltB);
2   input [3:0] A, B;
3   output reg AeqB, AgtB, AltB;
4
5   always @ (A, B)
6   begin
7     AeqB = 0;
8     AgtB = 0;
9     AltB = 0;
10    if (A == B)
11      AeqB = 1;
12    else if (A > B)
13      AgtB = 1;
14    else
15      AltB = 1;
16  end
17
18 endmodule
```

# Comparador por subtração

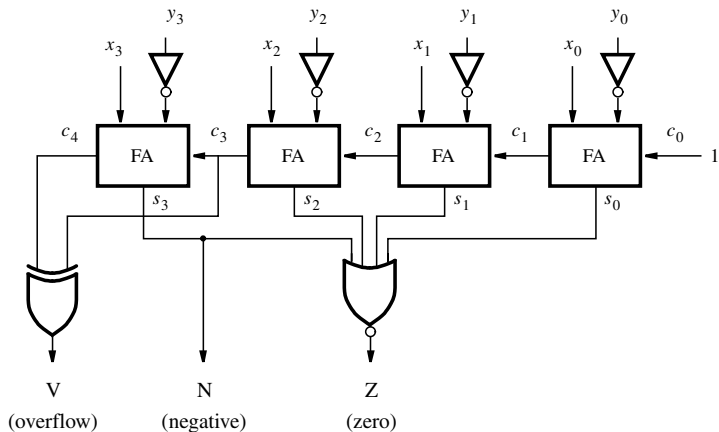

**Figure 3.45** A comparator circuit.

$$X < Y \iff N \oplus V$$

$$X = Y \iff Z$$

$$X \leq Y \iff (N \oplus V) + Z$$


## figure3.46.v

```
1  module comparator (X, Y, V, N, Z);
2      input  [3:0] X, Y;
3      output V, N, Z;
4      wire  [3:0] S;
5      wire  [4:1] C;
6
7      fulladd stage0 (1'b1, X[0], ~Y[0], S[0], C[1]);
8      fulladd stage1 (C[1], X[1], ~Y[1], S[1], C[2]);
9      fulladd stage2 (C[2], X[2], ~Y[2], S[2], C[3]);
10     fulladd stage3 (C[3], X[3], ~Y[3], S[3], C[4]);
11     assign V = C[4] ^ C[3];
12     assign N = S[3];
13     assign Z = !S;
14
15 endmodule
16
17 module fulladd (Cin, x, y, s, Cout);
18     input Cin, x, y;
19     output s, Cout;
20
21     assign s = x ^ y ^ Cin,
22            Cout = (x & y) | (x & Cin) | (y & Cin);
23
24 endmodule
```

## figure3.47.v

```
1 module comparator (X, Y, V, N, Z);
2   parameter n = 32;
3   input [n-1:0] X, Y;
4   output reg V, N, Z;
5   reg [n-1:0] S;
6   reg [n:0] C;
7   integer k;
8
9   always @(X, Y)
10  begin
11      C[0] = 1'b1;
12      for (k = 0; k < n; k = k + 1)
13          begin
14              S[k] = X[k] ^ ~Y[k] ^ C[k];
15              C[k+1] = (X[k] & ~Y[k]) | (X[k] & C[k]) | (~Y[k] & C[k]);
16          end
17      V = C[n] ^ C[n-1];
18      N = S[n-1];
19      Z = !S;
20  end
21
22 endmodule
```

# Deslocamento (*shift*)

 

**Figure 4.50** A shifter circuit.

## figure4.53.v

```
1 module shifter (W, Shift, Y , k);
2   input [3:0] W;
3   input Shift;
4   output reg [3:0] Y;
5   output reg k;
6
7   always @(W, Shift)
8   begin
9       if (Shift)
10      begin
11          Y[3] = 0;
12          Y[2:0] = W[3:1];
13          k = W[0];
14      end
15      else
16      begin
17          Y = W;
18          k = 0;
19      end
20  end
21
22 endmodule
```


## figure4.54.v

```
1 module shifter (W, Shift, Y , k);
2   input [3:0] W;
3   input Shift;
4   output reg [3:0] Y;
5   output reg k;
6
7   always @(W, Shift)
8   begin
9       if (Shift)
10        begin
11            Y = W >> 1;
12            k = W[0];
13        end
14    else
15        begin
16            Y = W;
17            k = 0;
18        end
19    end
20
21 endmodule
```

# Deslocamento (*rotate*)

$s_1$	$s_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	$w_3$	$w_2$	$w_1$	$w_0$
0	1	$w_0$	$w_3$	$w_2$	$w_1$
1	0	$w_1$	$w_0$	$w_3$	$w_2$
1	1	$w_2$	$w_1$	$w_0$	$w_3$

(a) Truth table

 

(b) Circuit

**Figure 4.51** A barrel shifter circuit.



## figure4.55.v

```
1 module barrel (W, S, Y);  
2     input [3:0] W;  
3     input [1:0] S;  
4     output [3:0] Y;  
5     wire [3:0] T;  
6  
7     assign {T, Y} = {W, W} >> S;  
8  
9 endmodule
```

**Table 4.1** The functionality of the 74381 ALU.

Operation	Inputs			Outputs F
	$s_2$	$s_1$	$s_0$	
Clear	0	0	0	0 0 0 0
B − A	0	0	1	$B - A$
A − B	0	1	0	$A - B$
ADD	0	1	1	$A + B$
XOR	1	0	0	$A \text{ XOR } B$
OR	1	0	1	$A \text{ OR } B$
AND	1	1	0	$A \text{ AND } B$
Preset	1	1	1	1 1 1 1

**Table 4.1** The functionality of the 74381 ALU.

Operation	Inputs $s_2 s_1 s_0$	Outputs $F$
Clear	0 0 0	0 0 0 0
B−A	0 0 1	$B - A$
A−B	0 1 0	$A - B$
ADD	0 1 1	$A + B$
XOR	1 0 0	$A \oplus B$
OR	1 0 1	$A \vee B$
AND	1 1 0	$A \wedge B$
Preset	1 1 1	1 1 1 1

```

1 // 74381 ALU
2 module alu (S, A, B, F);
3     input [2:0] S;
4     input [3:0] A, B;
5     output reg [3:0] F;
6
7     always @(S, A, B)
8         case (S)
9             0: F = 4'b0000;
10            1: F = B - A;
11            2: F = A - B;
12            3: F = A + B;
13            4: F = A ^ B;
14            5: F = A | B;
15            6: F = A & B;
16            7: F = 4'b1111;
17        endcase
18
19 endmodule

```

# Operadores em Verilog (1/2)

**Table 4.2** Verilog operators.

Operator type	Operator symbols	Operation performed	Number of operands
Bitwise	$\sim$	1's complement	1
	$\&$	Bitwise AND	2
	$ $	Bitwise OR	2
	$\wedge$	Bitwise XOR	2
	$\sim \wedge$ or $\wedge \sim$	Bitwise XNOR	2
Logical	$!$	NOT	1
	$\&\&$	AND	2
	$  $	OR	2
Reduction	$\&$	Reduction AND	1
	$\sim \&$	Reduction NAND	1
	$ $	Reduction OR	1
	$\sim  $	Reduction NOR	1
	$\wedge$	Reduction XOR	1
	$\sim \wedge$ or $\wedge \sim$	Reduction XNOR	1

■ ■ ■

## Operadores em Verilog (2/2)

■ ■ ■


Arithmetic	+	Addition	2
	-	Subtraction	2
	-	2's complement	1
	*	Multiplication	2
	/	Division	2
Relational	>	Greater than	2
	<	Less than	2
	>=	Greater than or equal to	2
	<=	Less than or equal to	2
Equality	==	Logical equality	2
	!=	Logical inequality	2
Shift	>>	Right shift	2
	<<	Left shift	2
Concatenation	{,}	Concatenation	Any number
Replication	{{}}	Replication	Any number
Conditional	?:	Conditional	3

# Precedencia dos Operadores em Verilog

**Table 4.3** Precedence of Verilog operators.


Operator type	Operator symbols	Precedence
Complement	! ~ -	Highest precedence
Arithmetic	* / + -	
Shift	<< >>	
Relational	< <= > >=	
Equality	== !=	
Reduction	& ~& & ~^   ~	
Logical	&& 	
Conditional	?:	Lowest precedence

# Perigo!: Especificação Incompleta

 

```
1 module mux3to1(a, b, c, sel, out);  
2   input [1:0] sel;  
3   input a, b, c;  
4   output out;  
5   reg out;  
6  
7   always @(a or b or c or sel)  
8   begin  
9       case (sel)  
10          2'b00: out = a;  
11          2'b01: out = b;  
12          2'b10: out = c;  
13      endcase  
14  end  
15 endmodule
```

# Perigo!: Especificação Incompleta

 




# Evitando a Especificação Incompleta

```
1  always @(a or b or c or sel)
2  begin
3      out = 1'bx
4      case (sel)
5          2'b00: out = a;
6          2'b01: out = b;
7          2'b10: out = c;
8      endcase
9  end
```


```
1  always @(a or b or c or sel)
2  begin
3      case (sel)
4          2'b00: out = a;
5          2'b01: out = b;
6          2'b10: out = c;
7          default: out = 1'bx
8      endcase
9  end
```

# Perigo!: Prioridade Indesejada

 


```
1 module binary_encoder(i, e);
2     input [3:0] i;
3     output [1:0] e;
4     reg e;
5
6     always @(i)
7     begin
8         if (i[0])
9             e = 2'b00;
10        else if (i[1])
11            e = 2'b01;
12        else if (i[2])
13            e = 2'b10;
14        else if (i[3])
15            e = 2'b11;
16        else
17            e = 2'bxx;
18    end
19 endmodule
```

# Perigo!: Prioridade Indesejada

 

# Evitando Prioridade Indesejada

 

```
1  module binary_encoder(i, e);
2      input  [3:0] i;
3      output [1:0] e;
4      reg e;
5
6      always @(i)
7      begin
8          if (i == 4'b0001)
9              e = 2'b00;
10         else if (i == 4'b0010)
11             e = 2'b01;
12         else if (i == 4'b0100)
13             e = 2'b10;
14         else if (i == 4'b1000)
15             e = 2'b11;
16         else
17             e = 2'bxx;
18     end
19 endmodule
```

# Bibliografia

- Brown, S. & Vranesic, Z. - Fundamentals of Digital Logic with Verilog Design, 3rd Ed., Mc Graw Hill, 2009

# Lógica Digital (1001351)

## Outros Circuitos Combinacionais

Prof. Edilson Kato

[kato@ufscar.br](mailto:kato@ufscar.br)

Prof. Maurício Figueiredo

[mauricio@ufscar.br](mailto:mauricio@ufscar.br)

Prof. Ricardo Menotti

[menotti@ufscar.br](mailto:menotti@ufscar.br)

Prof. Roberto Inoue

[rsinoue@ufscar.br](mailto:rsinoue@ufscar.br)

Departamento de Computação  
Universidade Federal de São Carlos

Atualizado em: 18 de abril de 2019

