

Lógica Digital (1001351)

Circuitos Sequenciais: Registradores

Prof. Edilson Kato
kato@ufscar.br

Prof. Maurício Figueiredo
mauricio@ufscar.br

Prof. Ricardo Menotti
menotti@ufscar.br

Prof. Roberto Inoue
rsinoue@ufscar.br

Departamento de Computação
Universidade Federal de São Carlos

Atualizado em: 11 de maio de 2019




Objetivos

Nesta aula vamos aprender sobre:

- ▶ Registradores, os quais armazenam vários bits;
- ▶ Registradores de deslocamento;
- ▶ Contadores de vários tipos.

Registrador de deslocamento

 

(a) Circuit

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

(b) A sample sequence

Figure 5.17 A simple shift register.

Registrador de deslocamento com carga paralela



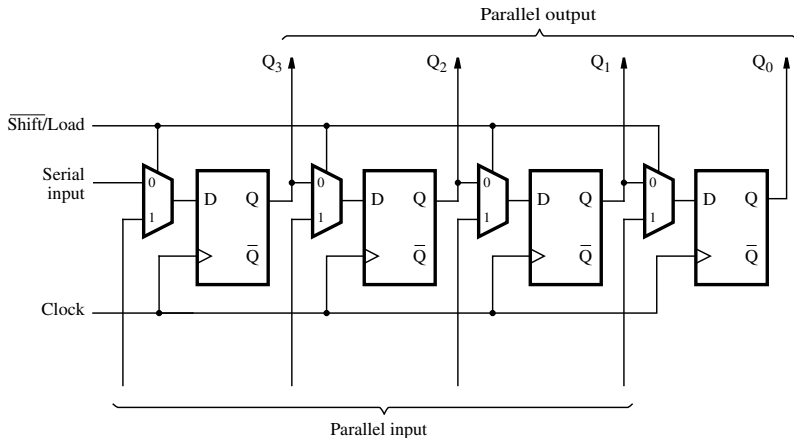


Figure 5.18 Parallel-access shift register.

Contador de três bits

 


(a) Circuit

 


(b) Timing diagram

Figure 5.19 A three-bit up-counter.

Contador de três bits (decremento)

 

(a) Circuit

 

(b) Timing diagram

Figure 5.20 A three-bit down-counter.

Table 5.1 Derivation of the synchronous up-counter.

Clock cycle	Q ₂	Q ₁	Q ₀	
0	0	0	0	
1	0	0	1	
2	0	1	0	← Q ₁ changes
3	0	1	1	
4	1	0	0	← Q ₂ changes
5	1	0	1	
6	1	1	0	
7	1	1	1	
8	0	0	0	

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$

$$T_3 = Q_0 Q_1 Q_2$$


.

.


.

$$T_n = Q_0 Q_1 \dots Q_{n-1}$$

Contador de 4 bits síncrono

 

(a) Circuit

 

(b) Timing diagram

Figure 5.21 A four-bit synchronous up-counter.

Contador de 4 bits síncrono com *enable*

 


Figure 5.22 Inclusion of Enable and Clear capability.

Contador com carga paralela



 


Figure 5.24 A counter with parallel-load capability.

Contador módulo-6 com reset síncrono

 


(a) Circuit

 


(b) Timing diagram

Figure 5.25 A modulo-6 counter with synchronous reset.

Contador módulo-6 com reset assíncrono

 

(a) Circuit

 

(b) Timing diagram

Figure 5.26 A modulo-6 counter with asynchronous reset.

Contador BCD de dois dígitos



 


Figure 5.27 A two-digit BCD counter.

Contador em anel

 

(a) An n -bit ring counter

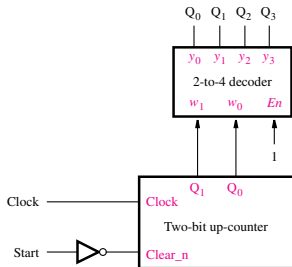

(b) A four-bit ring counter

Figure 5.28 Ring counter.

Contador Johnson

 


Figure 5.29 Johnson counter.

Bibliografia

- ▶ Brown, S. & Vranesic, Z. - Fundamentals of Digital Logic with Verilog Design, 3rd Ed., Mc Graw Hill, 2009
- ▶ <https://tams-www.informatik.uni-hamburg.de/applets/hades/>

Lógica Digital (1001351)

Circuitos Sequenciais: Registradores

Prof. Edilson Kato
kato@ufscar.br

Prof. Maurício Figueiredo
mauricio@ufscar.br

Prof. Ricardo Menotti
menotti@ufscar.br

Prof. Roberto Inoue
rsinoue@ufscar.br

Departamento de Computação
Universidade Federal de São Carlos

Atualizado em: 11 de maio de 2019

